

COL216 Assignment 2.3

Chinmay Mittal

February 2022

1 Introduction

The single cycle design made in the previous stage will be changed to a multi-cycle design in this stage.

Memory

The Data Memory and the Program Memory are combined into one single component named the memory. The memory has been modelled as a 128*32 array. I have assumed that the program memory will occupy the starting addresses in the memory and is expected to be initialize in the memory itself.


PC

PC is no longer handling computation for the next address, which is now be handled by the ALU and additional multiplexers logic. ALU computes word address which is changed to byte addressed before being stored into PC, which is now clocked and has a write enable signal PW.


FSM

Separate component to handle the control logic for the multi-cycle design, receives information about the signal and produces the corresponding control signals dependent on the current state. The current state is maintained as a an enumerated datatype, which changes based on the instruction on the clock rising edge. An asynchronous reset is also present

Circuit Diagram

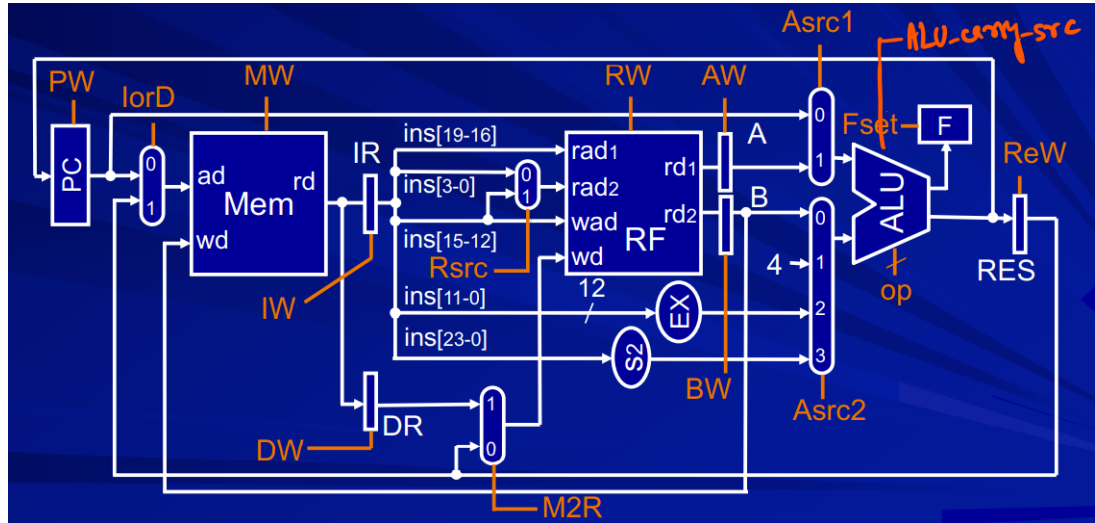

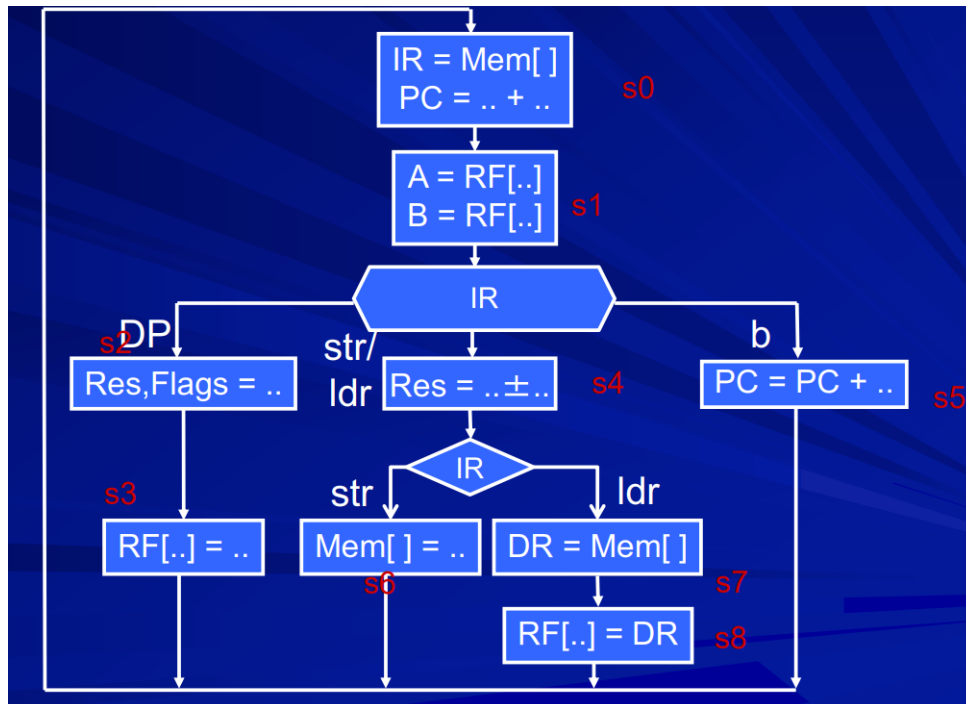
State Transition Diagram for FSM controller




Design Choices

- A new enumerated data type is created to hold the state of the FSM ($s0 \dots s8$)
- The FSM is separated into a component, which receives information about the instruction and produces control signals. The states change on the rising edge of the clock and also have an asynchronous reset to set the state to $s0$
- In each state appropriate control signals are set for the registers which means that the registers will be set and available at the rising edge of the next cycle.
- To produce next address ALU processes the PC has a word address and either adds (1) or the (branch offset and 1) , the later is achieved by setting the ALU operation to adc and setting the carry in to one.
- An additional Fset, signal has been added to the Flag module because Flags are not expected to be set in every iteration.

FSM circuit diagram

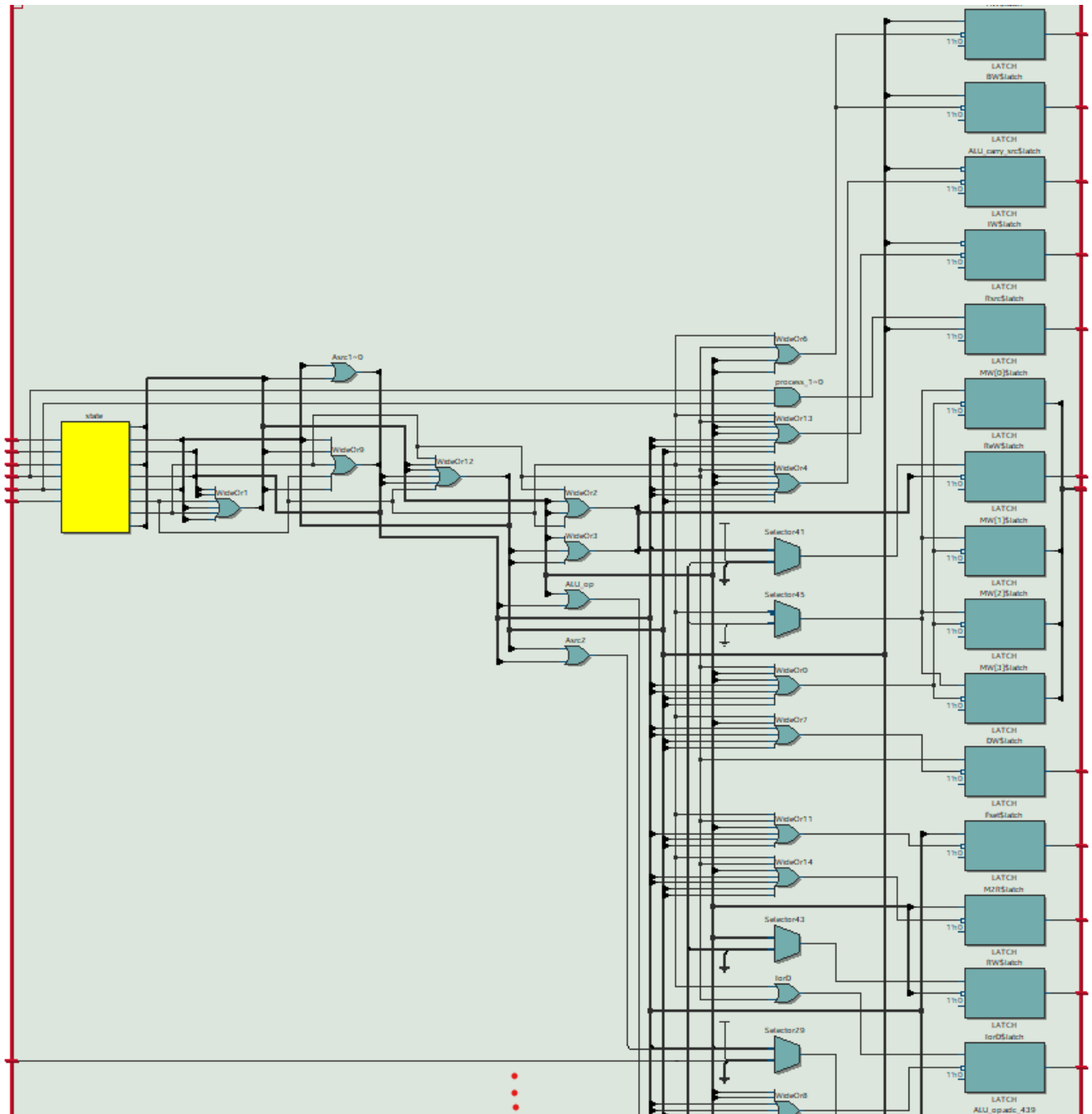

Processor circuit diagram

 

Program Testing 1


The two programs used in the previous assignment are used for testing but some modifications are made, in the first program the load/store address is changed to the 32 to avoid conflicting with the program instructions (both in the same memory) The EP wave generated is as follows and is tested for different signal values in the processor


Program Testing 2

The second program is modified so that the loop runs for a smaller number of iterations by changing the compare instruction to (cmp r1 , #2) as follows,

```
22 signal MEMORY : MEM := ( 0 => X"E3A00000",
23 1 => X"E3A01000",
24 2 => X"E0800001",
25 3 => X"E2811001",
26 4 => X"E3510002", ←
27 5 => X"1AFFFFFB",
28 others => X"00000000"
```

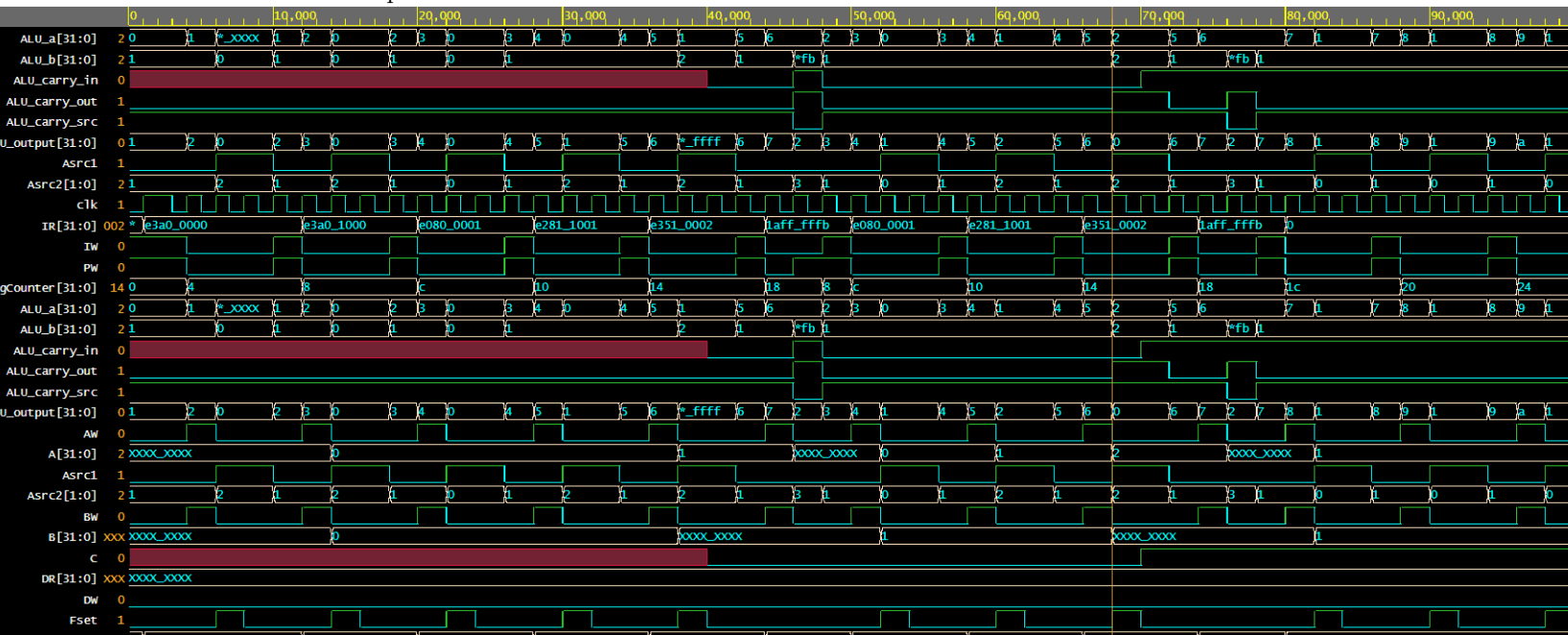The EP wave generated is as follows and is tested for different signal values in the processor



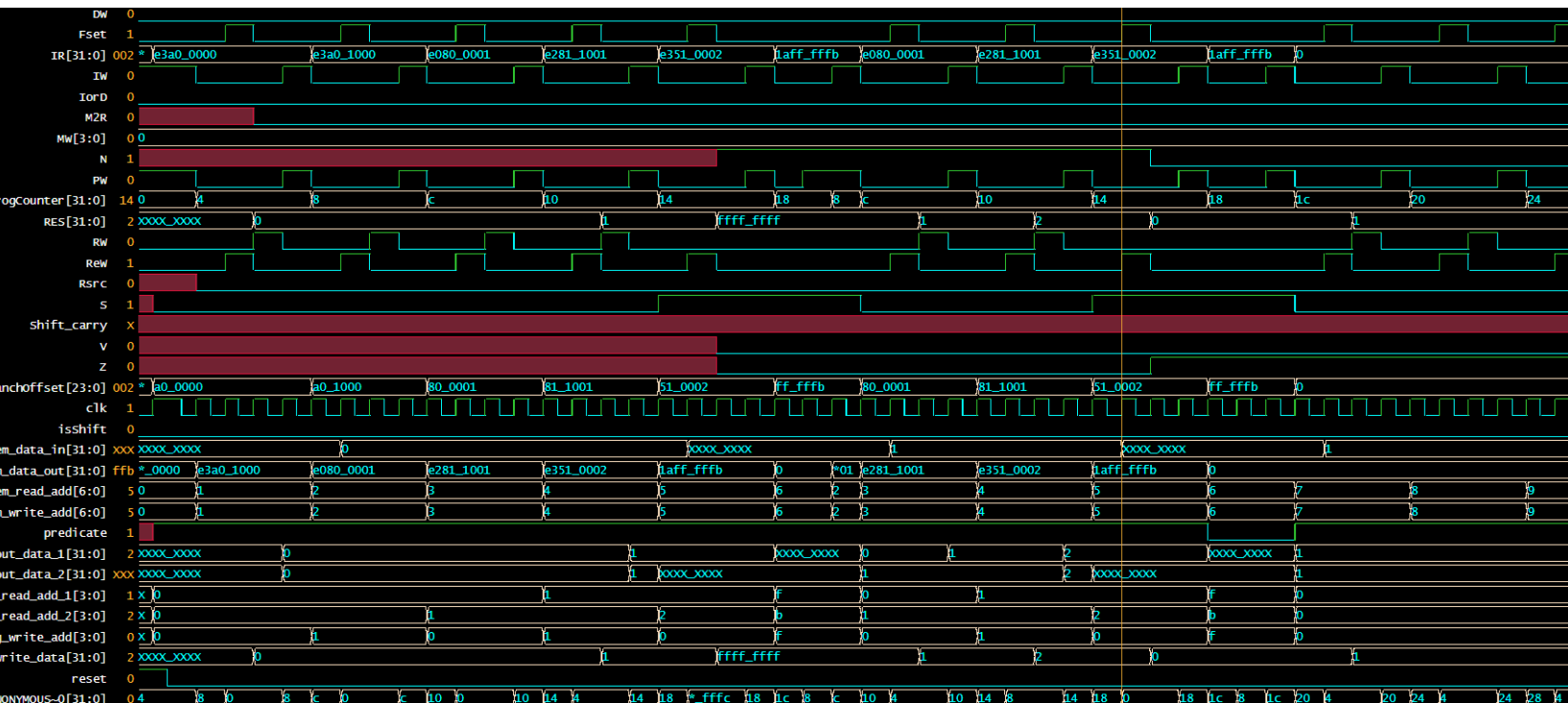

Resource Utilization for FSM

```
# Info: *****
# Info: Device Utilization for 7A100TCSG324
# Info: *****
# Info: Resource                                Used    Avail    Utilization
# Info: -----
# Info: I/Os                                67       210      31.90%
# Info: Global Buffers                      1        32       3.12%
# Info: LUTs                               26      63400    0.04%
# Info: CLB Slices                          5      15850    0.03%
# Info: Dffs or Latches                     40     126800  0.03%
# Info: Block RAMs                          0        135    0.00%
# Info: DSP48E1s                            0        240    0.00%
# Info: -----
```

Note

I forgot to mention in the last report, that the extra credit day was utilized in Assignment 2.2.